

ELECTRICAL MACHINES, DRIVES, AND POWER SYSTEMS

SIXTH EDITION 2006

TABLE OF CONTENTS

PART I. FUNDAMENTALS

1. UNITS, 3
 - 1.0 Introduction 3
 - 1.1 Systems of units 3
 - 1.2 Getting used to SI 4
 - 1.3 Base and derived units of the SI 4
 - 1.4 Definitions of base units 5
 - 1.5 Definitions of derived units 5
 - 1.6 Multiples and submultiples of SI units 7
 - 1.7 Commonly used units 7
 - 1.8 Conversion charts and their use 8
 - 1.9 The per-unit system of measurement 9
 - 1.10 Per-unit system with one base 10
 - 1.11 Per-unit system with two bases 11
 - Questions and Problems 12
2. FUNDAMENTALS OF ELECTRICITY,
MAGNETISM AND CIRCUITS 15
 - 2.0 Introduction 15
 - 2.1 Conventional and electron current flow 15
 - 2.2 Distinction between sources and loads 16
 - 2.3 Sign notation 17
 - 2.4 Double-subscript notation for voltages 17
 - 2.5 Sign notation for voltages 17
 - 2.6 Graph of an alternating voltage 18
 - 2.7 Positive and negative currents 19
 - 2.8 Sinusoidal voltage 19
 - 2.9 Converting cosine functions into sine functions 20
 - 2.10 Effective value of an ac voltage 20
 - 2.11 Phasor representation 21
 - 2.12 Harmonics 23
 - 2.13 Energy in an inductor 25
 - 2.14 Energy in a capacitor 25
 - 2.15 Some useful equations 26
 - ELECTROMAGNETISM
 - 2.16 Magnetic field intensity H and flux density B 27
 - 2.17 B - H curve of vacuum 27
 - 2.18 B - H curve of a magnetic material 27
 - 2.19 Determining the relative permeability 28
 - 2.20 Faraday's law of electromagnetic induction 29
 - 2.21 Voltage induced in a conductor 30
 - 2.22 Lorentz force on a conductor 31
 - 2.23 Direction of the force acting on a straight conductor 31
 - 2.24 Residual flux density and coercive force 32
 - 2.25 Hysteresis loop 33
 - 2.26 Hysteresis loss 33
 - 2.27 Hysteresis losses caused by rotation 33
 - 2.28 Eddy currents 34
 - 2.29 Eddy currents in a stationary iron core 35
 - 2.30 Eddy-current losses in a revolving core 35
 - 2.31 Current in an inductor 36
 - CIRCUITS AND EQUATIONS
 - 2.32 Kirchhoff's voltage law 40
 - 2.33 Kirchhoff's voltage law and double-subscript notation 40
 - 2.34 Kirchhoff's current law 41
 - 2.35 Currents, impedances, and associated voltages 41
 - 2.36 Kirchhoff's laws and ac circuits 43
 - 2.37 KVL and sign notation 43
 - 2.38 Solving ac and dc circuits with sign notation 44
 - 2.39 Circuits and hybrid notation 45

Questions and Problems 46

3. FUNDAMENTALS OF MECHANICS AND HEAT 50

- 3.0 Introduction 50
 - 3.1 Force 50
 - 3.2 Torque 51
 - 3.3 Mechanical work 51
 - 3.4 Power 52
 - 3.5 Power of a motor 52
 - 3.6 Transformation of energy 53
 - 3.7 Efficiency of a machine 53
 - 3.8 Kinetic energy of linear motion 54
 - 3.9 Kinetic energy of rotation, moment of inertia 54
 - 3.10 Torque, inertia and change in speed 57
 - 3.11 Speed of a motor/load system 57
 - 3.12 Power flow in a mechanically coupled system 58
 - 3.13 Motor driving a load having inertia 58
 - 3.14 Electric motors driving linear motion loads 59
 - 3.15 Heat and temperature 60
 - 3.16 Temperature scales 61
 - 3.17 Heat required to raise the temperature of a body 61
 - 3.18 Transmission of heat 62
 - 3.19 Heat transfer by conduction 62
 - 3.20 Heat transfer by convection 63
 - 3.21 Calculating the losses by convection 63
 - 3.22 Heat transfer by radiation 64
 - 3.23 Calculating radiation losses 64
- Questions and Problems 65

PART II. ELECTRICAL MACHINES AND TRANSFORMERS

4. DIRECT-CURRENT GENERATORS 71

- 4.0 Introduction 71
- 4.1 Generating an ac voltage 71
- 4.2 Direct-current generator 72

- 4.3 Difference between ac and dc generators 73
 - 4.4 Improving the waveshape 73
 - 4.5 Induced voltage 75
 - 4.6 Neutral zones 76
 - 4.7 Value of the induced voltage 76
 - 4.8 Generator under load: the energy conversion process 77
 - 4.9 Armature reaction 77
 - 4.10 Shifting the brushes to improve commutation 78
 - 4.11 Commutating poles 79
 - 4.12 Separately excited generator 79
 - 4.13 No-load operation and saturation curve 79
 - 4.14 Shunt generator 80
 - 4.15 Controlling the voltage of a shunt generator 81
 - 4.16 Equivalent circuit 82
 - 4.17 Separately excited generator under load 82
 - 4.18 Shunt generator under load 83
 - 4.19 Compound generator 83
 - 4.20 Differential compound generator 84
 - 4.21 Load characteristics 84
 - 4.22 Generator specifications 84
- CONSTRUCTION OF DIRECT-CURRENT GENERATORS
- 4.23 Field 84
 - 4.24 Armature 85
 - 4.25 Commutator and brushes 86
 - 4.26 Details of a multipole generator 88
 - 4.27 The ideal commutation process 91
 - 4.28 The practical commutation process 92
- Questions and Problems 94

5. DIRECT-CURRENT MOTORS 96

- 5.0 Introduction 96
- 5.1 Counter-electromotive force (cemf) 96
- 5.2 Acceleration of the motor 97
- 5.3 Mechanical power and torque 98
- 5.4 Speed of rotation 100

- 5.5 Armature speed control 101
 - 5.6 Field speed control 102
 - 5.7 Shunt motor under load 103
 - 5.8 Series motor 104
 - 5.9 Series motor speed control 105
 - 5.10 Applications of the series motor 106
 - 5.11 Compound motor 106
 - 5.12 Reversing the direction of rotation 107
 - 5.13 Starting a shunt motor 108
 - 5.14 Face-plate starter 108
 - 5.15 Stopping a motor 109
 - 5.16 Dynamic braking 109
 - 5.17 Plugging 110
 - 5.18 Dynamic braking and mechanical time constant 111
 - 5.19 Armature reaction 113
 - 5.20 Flux distortion due to armature reaction 113
 - 5.21 Commutating poles 113
 - 5.22 Compensating winding 114
 - 5.23 Basics of variable speed control 114
 - 5.24 Permanent magnet motors 117
 - Questions and Problems 118
6. EFFICIENCY AND HEATING OF ELECTRICAL MACHINES 120
- 6.0 Introduction 120
 - 6.1 Mechanical losses 120
 - 6.2 Electrical losses 120
 - 6.3 Losses as a function of load 123
 - 6.4 Efficiency curve 123
 - 6.5 Temperature rise 125
 - 6.6 Life expectancy of electric equipment 126
 - 6.7 Thermal classification of insulators 126
 - 6.8 Maximum ambient temperature and hot-spot temperature rise 127
 - 6.9 Temperature rise by the resistance method 129
 - 6.10 Relationship between the speed and size of a machine 130
 - Questions and Problems 131
7. ACTIVE, REACTIVE, AND APPARENT POWER 134
- 7.0 Introduction 134
 - 7.1 Instantaneous power 134
 - 7.2 Active power 136
 - 7.3 Reactive power 137
 - 7.4 Definition of reactive load and reactive source 138
 - 7.5 The capacitor and reactive power 139
 - 7.6 Distinction between active and reactive power 140
 - 7.7 Combined active and reactive loads: apparent power 141
 - 7.8 Relationship between P , Q , and S 141
 - 7.9 Power factor 143
 - 7.10 Power triangle 144
 - 7.11 Further aspects of sources and loads 144
 - 7.12 Systems comprising several loads 146
 - 7.13 Reactive power without magnetic fields 148
 - 7.14 Solving AC circuits using the power triangle method 148
 - 7.15 Power and vector notation 151
 - 7.16 Rules on sources and loads (sign notation) 154
 - 7.17 Rules on sources and loads (double subscript notation) 154
 - Questions and Problems 155
8. THREE-PHASE CIRCUITS 158
- 8.0 Introduction 158
 - 8.1 Polyphase systems 158
 - 8.2 Single-phase generator 159
 - 8.3 Power output of a single-phase generator 160
 - 8.4 Two-phase generator 160
 - 8.5 Power output of a 2-phase generator 161
 - 8.6 Three-phase generator 162
 - 8.7 Power output of a 3-phase generator 162
 - 8.8 Wye connection 164
 - 8.9 Voltage relationships 165

- 8.10 Delta connection 167
- 8.11 Power transmitted by a 3-phase line 168
- 8.12 Active, reactive and apparent power in 3-phase circuits 169
- 8.13 Solving 3-phase circuits 170
- 8.14 Industrial loads 171
- 8.15 Phase sequence 174
- 8.16 Determining the phase sequence 175
- 8.17 Power measurement in ac circuits 176
- 8.18 Power measurement in 3-phase, 3-wire circuits 176
- 8.19 Power measurement in 3-phase, 4- wire circuits 177
- 8.20 Varmeter 177
- 8.21 A remarkable single-phase to 3-phase transformation 178
- Questions and Problems 180
- 9. THE IDEAL TRANSFORMER 183
 - 9.0 Introduction 183
 - 9.1 Voltage induced in a coil 183
 - 9.2 Applied voltage and induced voltage 184
 - 9.3 Elementary transformer 185
 - 9.4 Polarity of a transformer 186
 - 9.5 Properties of polarity marks 186
 - 9.6 Ideal transformer at no-load; voltage ratio 187
 - 9.7 Ideal transformer under load; current ratio 188
 - 9.8 Circuit symbol for an ideal transformer 191
 - 9.9 Impedance ratio 191
 - 9.10 Shifting impedances from secondary to primary and vice versa 192
 - Questions and Problems 195
- 10. PRACTICAL TRANSFORMERS 197
 - 10.0 Introduction 197
 - 10.1 Ideal transformer with an imperfect core 197
 - 10.2 Ideal transformer with loose coupling 199
 - 10.3 Primary and secondary leakage reactance 200
 - 10.4 Equivalent circuit of a practical transformer 202
 - 10.5 Construction of a power transformer 203
 - 10.6 Standard terminal markings 204
 - 10.7 Polarity tests 204
 - 10.8 Transformer taps 205
 - 10.9 Losses and transformer rating 206
 - 10.10 No-load saturation curve 206
 - 10.11 Cooling methods 207
 - 10.12 Simplifying the equivalent circuit 209
 - 10.13 Voltage regulation 211
 - 10.14 Measuring transformer impedances 212
 - 10.15 Introducing the per unit method 215
 - 10.16 Impedance of a transformer 216
 - 10.17 Typical per-unit impedances 216
 - 10.18 Transformers in parallel 219
 - Questions and Problems 221
- 11. SPECIAL TRANSFORMERS 225
 - 11.0 Introduction 225
 - 11.1 Dual-voltage distribution transformer 225
 - 11.2 Autotransformer 226
 - 11.3 Conventional transformer connected as an autotransformer 228
 - 11.4 Voltage transformers 230
 - 11.5 Current transformers 231
 - 11.6 Opening the secondary of a CT can be dangerous 233
 - 11.7 Toroidal current transformers 234
 - 11.8 Variable autotransformer 235
 - 11.9 High-impedance transformers 236
 - 11.10 Induction heating transformers 237
 - 11.11 High-frequency transformers 238
 - Questions and Problems 241
- 12. THREE-PHASE TRANSFORMERS 243
 - 12.0 Introduction 243
 - 12.1 Basic properties of 3-phase transformer banks 243
 - 12.2 Delta-delta connection 244

- 12.3 Delta-wye connection 246
- 12.4 Wye-delta connection 247
- 12.5 Wye-wye connection 248
- 12.6 Open-delta connection 248
- 12.7 Three-phase transformers 249
- 12.8 Step-up and step-down autotransformer 251
- 12.9 Phase-shift principle 253
- 12.10 Three-phase to 2-phase transformation 254
- 12.11 Phase-shift transformer 256
- 12.12 Calculations involving 3-phase transformers 258
- 12.13 Polarity marking of 3-phase transformers 260
- Questions and Problems 261
- 13. THREE-PHASE INDUCTION MOTORS 263
 - 13.0 Introduction 263
 - 13.1 Principal components 263
 - 13.2 Principle of operation 264
 - 13.3 The rotating field 265
 - 13.4 Direction of rotation 270
 - 13.5 Number of poles–synchronous speed 271
 - 13.6 Starting characteristics of a squirrel-cage motor 273
 - 13.7 Acceleration of the rotor–slip 274
 - 13.8 Motor under load 274
 - 13.9 Slip 274
 - 13.10 Voltage and frequency induced in the rotor 275
 - 13.11 Characteristics of squirrel-cage induction motors 276
 - 13.12 Estimating the currents in an induction motor 277
 - 13.13 Active power flow 278
 - 13.14 Torque versus speed curve 281
 - 13.15 Effect of rotor resistance 282
 - 13.16 Wound-rotor motor 284
 - 13.17 Three-phase windings 285
 - 13.18 Sector motor 288
 - 13.19 Linear induction motor 289
 - 13.20 Traveling waves 291
 - 13.21 Properties of a linear induction motor 291
 - 13.22 Magnetic levitation 293
 - Questions and Problems 295
 - The Doubly-Fed Induction Machine**
 - 13.23 Doubly-fed wound-rotor motor (speed relationships), 295
 - 13.24 Doubly-fed wound-rotor motor (power relationships at subsynchronous speed), 297
 - 13-25 Doubly-fed wound-rotor motor (power relationships at supersynchronous speed), 300
 - 13-26 Doubly-fed wound-rotor generator, 300
 - Questions and Problems
- 14. SELECTION AND APPLICATION OF THREE-PHASE INDUCTION MOTORS 299
 - 14.0 Introduction 307
 - 14.1 Standardization and classification of induction motors 307
 - 14.2 Classification according to environment and cooling methods 307
 - 14.3 Classification according to electrical and mechanical properties 309
 - 14.4 Choice of motor speed 311
 - 14.5 Two-speed motors 311
 - 14.6 Induction motor characteristics under various load conditions 313
 - 14.7 Starting an induction motor 316
 - 14.8 Plugging an induction motor 316
 - 14.9 Braking with direct current 317
 - 14.10 Abnormal conditions 318
 - 14.11 Mechanical overload 318
 - 14.12 Line voltage changes 318
 - 14.13 Single-phasing 318
 - 14.14 Frequency variation 319
 - 14.15 Induction motor operating as a generator 319
 - 14.16 Complete torque-speed characteristic of an induction machine 322
 - 14.17 Features of a wound-rotor induction motor 323
 - 14.18 Start-up of high-inertia loads 323
 - 14.19 Variable-speed drives 323

- 14.20 Frequency converter 323
- Questions and Problems 326
- 15. EQUIVALENT CIRCUIT OF THE INDUCTION MOTOR 330
 - 15.0 Introduction 330
 - 15.1 The wound-rotor induction motor 330
 - 15.2 Power relationships 333
 - 15.3 Phasor diagram of the induction motor 334
 - 15.4 Breakdown torque and speed 335
 - 15.5 Equivalent circuit of two practical motors 335
 - 15.6 Calculation of the breakdown torque 336
 - 15.7 Torque-speed curve and other characteristics 337
 - 15.8 Properties of an asynchronous generator 338
 - 15.9 Tests to determine the equivalent circuit 339
 - Questions and Problems 341
- 16. SYNCHRONOUS GENERATORS 343
 - 16.0 Introduction 343
 - 16.1 Commercial synchronous generators 335
 - 16.2 Number of poles 335
 - 16.3 Main features of the stator 343
 - 16.4 Main features of the rotor 344
 - 16.5 Field excitation and exciters 350
 - 16.6 Brushless excitation 351
 - 16.7 Factors affecting the size of synchronous generators 352
 - 16.8 No-load saturation curve 353
 - 16.9 Synchronous reactance–equivalent circuit of an ac generator 354
 - 16.10 Determining the value of X_s 356
 - 16.11 Base impedance, per-unit X_s 357
 - 16.12 Short-circuit ratio 358
 - 16.13 Synchronous generator under load 358
 - 16.14 Regulation curves 360
 - 16.15 Synchronization of a generator 361
 - 16.16 Synchronous generator on an infinite bus 363
 - 16.17 Infinite bus–effect of varying the exciting current 363
 - 16.18 Infinite bus–effect of varying the mechanical torque 363
 - 16.19 Physical interpretation of alternator behavior 365
 - 16.20 Active power delivered by the generator 366
 - 16.21 Control of active power 367
 - 16.22 Transient reactance 367
 - 16.23 Power transfer between two sources 369
 - 16.24 Efficiency, power, and size of electrical machines 370
 - Questions and Problems 372
- 17. SYNCHRONOUS MOTORS 377
 - 17.0 Introduction 377
 - 17.1 Construction 378
 - 17.2 Starting a synchronous motor 380
 - 17.3 Pull-in torque 380
 - 17.4 Motor under load–general description 380
 - 17.5 Motor under load–simple calculations 381
 - 17.6 Power and torque 384
 - 17.7 Mechanical and electrical angles 385
 - 17.8 Reluctance torque 386
 - 17.9 Losses and efficiency of a synchronous motor 387
 - 17.10 Excitation and reactive power 388
 - 17.11 Power factor rating 389
 - 17.12 V-curves 390
 - 17.13 Stopping synchronous motors 391
 - 17.14 The synchronous motor versus the induction motor 393
 - 17.15 Synchronous capacitor 393
 - Questions and Problems 396
- 18. SINGLE-PHASE MOTORS 399
 - 18.0 Introduction 399
 - 18.1 Construction of a single-phase induction motor 399

18.2	Synchronous speed	401			
18.3	Torque-speed characteristic	402			
18.4	Principle of operation	402			
18.5	Locked-rotor torque	404			
18.6	Resistance split-phase motor	404			
18.7	Capacitor-start motor	406			
18.8	Efficiency and power factor of single-phase induction motors	407			
18.9	Vibration of single-phase motors	409			
18.10	Capacitor-run motor	410			
18.11	Reversing the direction of rotation	411			
18.12	Shaded-pole motor	411			
18.13	Universal motor	412			
18.14	Hysteresis motor	413			
18.15	Synchronous reluctance motor	415			
18.16	Synchro drive	416			
	EQUIVALENT CIRCUIT OF A SINGLE-PHASE MOTOR				
18.17	Magnetomotive force distribution	417			
18.18	Revolving mmfs in a single-phase motor	418			
18.19	Deducing the circuit diagram of a single-phase motor	419			
	Questions and Problems	422			
19.	STEPPER MOTORS	425			
19.0	Introduction	425			
19.1	Elementary stepper motor	425			
19.2	Effect of inertia	426			
19.3	Effect of a mechanical load	427			
19.4	Torque versus current	428			
19.5	Start-stop stepping rate	428			
19.6	Slew speed	429			
19.7	Ramping	430			
19.8	Types of stepper motors	430			
19.9	Motor windings and associated drives	432			
19.10	High-speed operation	435			
19.11	Modifying the time constant	436			
19.12	Bilevel drive	436			
19.13	Instability and resonance	442			
19.14	Stepper motors and linear drives	442			
	Questions and Problems	442			
	PART III. ELECTRICAL AND ELECTRONIC DRIVES				
20.	BASICS OF INDUSTRIAL MOTOR CONTROL	447			
20.0	Introduction	447			
20.1.	Control devices	448			
20.2.	Normally-open and normally-closed contacts	451			
20.3.	Relay coil exciting current	451			
20.4.	Control diagrams	453			
20.5.	Starting methods	454			
20.6.	Manual across-the-line starters	455			
20.7.	Magnetic across-the-line starters	456			
20.8.	Inching and jogging	458			
20.9.	Reversing the direction of rotation	459			
20.10	Plugging	461			
20.11	Reduced-voltage starting	462			
20.12	Primary resistance starting	462			
20.13	Autotransformer starting	463			
20.14	Other starting methods	468			
20.15	Cam switches	469			
	ELECTRIC DRIVES				
20.16	Fundamentals of electric drives	470			
20.17	Typical torque-speed curves	471			
20.18	Shape of the torque-speed curve	472			
20.19	Current-speed curves	474			
20.20	Regenerative braking	475			
	Questions and Problems	476			
21.	FUNDAMENTAL ELEMENTS OF POWER ELECTRONICS	480			
21.0	Introduction	480			
21.1	Potential level	480			
21.2	Voltage across some circuit elements	482			
	THE DIODE AND DIODE CIRCUITS				
21.3	The diode	483			
21.4	Main characteristics of a diode	484			
21.5	Battery charger with series resistor	484			

- 21.6 Battery charger with series inductor 486
- 21.7 Single-phase bridge rectifier 488
- 21.8 Filters 489
- 21.9 Three-phase, 3-pulse diode rectifier 491
- 21.10 Three-phase, 6-pulse rectifier 493
- 21.11 Effective line current, fundamental line current 497
- 21.12 Distortion power factor 498
- 21.13 Displacement power factor, total power factor 498
- 21.14 Harmonic content, THD 499
 - THE THYRISTOR
 - AND THYRISTOR CIRCUITS
- 21.15 The thyristor 500
- 21.16 Principles of gate firing 500
- 21.17 Power gain of a thyristor 502
- 21.18 Current interruption and forced commutation 503
- 21.19 Basic thyristor power circuits 504
- 21.20 Controlled rectifier supplying a passive load (Circuit 1, Table 21 D) 504
- 21.21 Controlled rectifier supplying an active load (Circuit 2, Table 21D) 505
- 21.22 Line-commutated inverter (Circuit 3, Table 21D) 506
- 21.23 AC static switch (Circuit 4, Table 21D) 508
- 21.24 Cycloconverter (Circuit 5, Table 21D) 509
- 21.25 Three-phase, 6-pulse controllable converter (Circuit 6, Table 21D) 510
- 21.26 Basic principle of operation 511
- 21.27 Three-phase, 6-pulse rectifier feeding an active load 512
- 21.28 Delayed triggering–rectifier mode 513
- 21.29 Delayed triggering–inverter mode 515
- 21.30 Triggering range 516
- 21.31 Equivalent circuit of a converter 517
- 21.32 Currents in a 3-phase, 6-pulse converter 519
- 21.33 Power factor 519
- 21.34 Commutation overlap 522
- 21.35 Extinction angle 522
- DC-TO-DC SWITCHING CONVERTERS
 - 21.36 Semiconductor switches 523
 - 21.37 DC-to-DC switching converter 525
 - 21.38 Rapid switching 527
 - 21.39 Impedance transformation 530
 - 21.40 Basic 2-quadrant dc-to-dc converter 530
 - 21.41 Two-quadrant electronic converter 533
 - 21.42 Four-quadrant dc-to-dc converter 534
 - 21.43 Switching losses 536
- DC-TO-AC SWITCHING CONVERTERS
 - 21.44 Dc-to-ac rectangular wave converter 537
 - 21.45 Dc-to-ac converter with pulse-width modulation 538
 - 21.46 Dc-to-ac sine wave converter 540
 - 21.47 Generating a sine wave 541
 - 21.48 Creating the PWM pulse train 542
 - 21.49 Dc-to-ac 3-phase converter 544
 - 21.50 The convwerter as a universal generator, 549
 - 21.50 Conclusion 550
 - Questions and Problems 550
- 22. ELECTRONIC CONTROL OF DIRECT-CURRENT MOTORS 555
 - 22.0 Introduction 555
 - 22.1 First quadrant speed control 555
 - 22.2 Two-quadrant control–field reversal 558
 - 22.3 Two-quadrant control–armature reversal 559
 - 22.4 Two-quadrant control–two converters 559
 - 22.5 Four-quadrant control–two converters with circulating current 560
 - 22.6 Two-quadrant control with positive torque 563
 - 22.7 Four-quadrant drive 563
 - 22.8 Six-pulse converter with freewheeling diode 565
 - 22.9 Half-bridge converter 570
 - 22.10 DC traction 572
 - 22.11 Motor drive using a dc-to-dc switching converter 574
 - 22.12 Introduction to brushless dc motors 565

- 22.13 Commutator replaced by reversing switches 580
- 22.14 Synchronous motor as a brushless dc machine 568
- 22.15 Standard synchronous motor and brushless dc machine 583
- 22.16 Practical application of a brushless dc motor 583
- Questions and Problems 585
- 23. ELECTRONIC CONTROL OF ALTERNATING CURRENT MOTORS 589
 - 23.0 Introduction 589
 - 23.1 Types of ac drives 589
 - 23.2 Synchronous motor drive using current-source dc link 591
 - 23.3 Synchronous motor and cycloconverter 594
 - 23.4 Cycloconverter voltage and frequency control 594
 - 23.5 Squirrel-cage induction motor with cycloconverter 596
 - 23.6 Squirrel-cage motor and static voltage controller 603
 - 23.7 Soft-starting cage motors 604
 - SELF-COMMUTATED INVERTERS
 - 23.8 Self-commutated inverters for cage motors 606
 - 23.9 Current-source self-commutated frequency converter (rectangular wave) 607
 - 23.10 Voltage-source self-commutated frequency converter (rectangular wave) 610
 - 23.11 Chopper speed control of a wound-rotor induction motor 611
 - 23.12 Recovering power in a wound-rotor induction motor 613
 - PULSE-WIDTH MODULATION DRIVES
 - 23.13 Review of pulse-width modulation 616
 - 23.14 Pulse-width modulation and induction motors 618
 - TORQUE AND SPEED CONTROL OF INDUCTION MOTORS
 - 23.15 Dc motor and flux orientation 618
 - 23.16 Slip speed, flux orientation, and torque 619
 - 23.17 Features of variable-speed control–constant torque mode 621
 - 23.18 Features of variable-speed control–constant horsepower mode 624
 - 23.19 Features of variable-speed control–generator mode 624
 - 23.20 Induction motor and its equivalent circuit 625
 - 23.21 Equivalent circuit of a practical motor 626
 - 23.22 Volts per hertz of a practical motor 627
 - 23.23 Speed and torque control of induction motors 628
 - 23.24 Carrier frequencies 629
 - 23.25 Dynamic control of induction motors 629
 - 23.26 Principle of flux vector control 616
 - 23.27 Variable-speed drive and electric traction 632
 - 23.28 Principal components 621
 - 23.29 Operating mode of the 3-phase converter 636
 - 23.30 Operating mode of the single-phase converter 638
 - 23.31 Conclusion 643
 - 23.32 Controlling the flux and torque by hysteresis, 644
 - 23.33 Controlling the speed, 644
 - 23.34 Producing a magnetic field in a 2-phase motor, 644
 - 23.35 Producing a rotating field, 647
 - 23.36 Controlling the magnetic flux, 648
 - 23.37 Controlling the speed of rotation, 650
 - 23.38 Programming logic of the switching procedure, 650
 - 23.39 Instantaneous slip and the production of torque, 652
 - 23.40 Control of 3-phase motors, 653
 - 23.41 Schematic diagram of a DTC, 655
 - 23.42 Conclusion, 656
 - Questions and Problems, 658

PART IV. ELECTRIC UTILITY POWER SYSTEMS

- 24. GENERATION OF ELECTRICAL ENERGY 665
 - 24.0 Introduction 635
 - 24.1 Demand of an electrical system 665
 - 24.2 Location of the generating station 667
 - 24.3 Types of generating stations 667
 - 24.4 Controlling the power balance between generator and load 668
 - 24.5 Advantage of interconnected systems 669
 - 24.6 Conditions during an outage 671
 - 24.7 Frequency and electric clocks 672
 - HYDROPOWER GENERATING STATIONS
 - 24.8 Available hydro power 672
 - 24.9 Types of hydropower stations 673
 - 24.10 Makeup of a hydropower plant 674
 - 24.11 Pumped-storage installations 676
 - THERMAL GENERATING STATIONS
 - 24.12 Makeup of a thermal generating station 678
 - 24.13 Turbines 680
 - 24.14 Condenser 680
 - 24.15 Cooling towers 680
 - 24.16 Boiler-feed pump 681
 - 24.17 Energy flow diagram for a steam plant 681
 - 24.18 Thermal stations and the environment 652
 - NUCLEAR GENERATING STATIONS
 - 24.19 Composition of an atomic nucleus; isotopes 685
 - 24.20 The source of uranium 685
 - 24.21 Energy released by atomic fission 686
 - 24.22 Chain reaction 686
 - 24.23 Types of nuclear reactors 687
 - 24.24 Example of a light-water reactor 688
 - 24.25 Example of a heavy-water reactor 689
 - 24.26 Principle of the fast breeder reactor 690
 - 24.27 Nuclear fusion 691
 - Wind-Generating Stations**
 - 24.28 Properties of the wind, 691
 - 24.29 Harnessing wind power, 693
 - 24.30 Wind turbine driving a dc generator, 693
 - 24.31 Turbine driving an asynchronous generator at constant speed, 693
 - 24.32 Turbine driving an asynchronous generator at variable speed, 694
 - 24.33 Turbine driving a doubly-fed induction generator, 695
 - 24.34 Turbine directly driving a permanent magnet alternator, 696
 - 24.35 Examples of wind-generating stations, 697
 - Questions and Problems, 700
- 25. TRANSMISSION OF ELECTRICAL ENERGY 706
 - 25.0 Introduction 706
 - 25.1 Principal components of a power distribution system 706
 - 25.2 Types of power lines 707
 - 25.3 Standard voltages 709
 - 25.4 Components of a HV transmission line 709
 - 25.5 Construction of a line 710
 - 25.6 Galloping lines 711
 - 25.7 Corona effect—radio interference 711
 - 25.8 Pollution 711
 - 25.9 Lightning strokes 712
 - 25.10 Lightning arresters on buildings 713
 - 25.11 Lightning and transmission lines 713
 - 25.12 Basic impulse insulation level (BIL) 714
 - 25.13 Ground wires 715
 - 25.14 Tower grounding 715
 - 25.15 Fundamental objectives of a transmission line 717
 - 25.16 Equivalent circuit of a line 718
 - 25.17 Typical impedance values 718
 - 25.18 Simplifying the equivalent circuit 720
 - 25.19 Voltage regulation and power-transmission capability of transmission lines 722
 - 25.20 Resistive line 722
 - 25.21 Inductive line 723

- 25.22 Compensated inductive line 725
- 25.23 Inductive line connecting two systems 727
- 25.24 Review of power transmission 728
- 25.25 Choosing the line voltage 729
- 25.26 Methods of increasing the power capacity 731
- 25.27 Extra-high-voltage lines 731
- 25.28 Power exchange between power centers 734
- 25.29 Practical example of power exchange 735
- Questions and Problems 737
- 26. DISTRIBUTION OF ELECTRICAL ENERGY 740
 - 26.0 Introduction 740
 - SUBSTATONS
 - 26.1 Substation equipment 740
 - 26.2 Circuit breakers 740
 - 26.3 Air-break switches 744
 - 26.4 Disconnecting switches 744
 - 26.5 Grounding switches 744
 - 26.6 Surge arresters 744
 - 26.7 Current-limiting reactors 747
 - 26.8 Grounding transformer 748
 - 26.9 Example of a substation 749
 - 26.10 Medium-voltage distribution 751
 - 26.11 Low-voltage distribution 751
 - PROTECTION OF MEDIUM-VOLTAGE DISTRIBUTION SYSTEMS
 - 26.12 Coordination of the protective devices 756
 - 26.13 Fused cutouts 757
 - 26.14 Reclosers 758
 - 26.15 Sectionalizers 758
 - 26.16 Review of MV protection 759
 - LOW-VOLTAGE DISTRIBUTION
 - 26.17 LV distribution system 759
 - 26.18 Grounding electrical installations 76
 - 26.19 Electric shock 761
 - 26.20 Grounding of 120 V and 240 V/120 V systems 762
 - 26.21 Equipment grounding 763
 - 26.22 Ground-fault circuit breaker 765
 - 26.23 Rapid conductor heating: I^2t factor 766
 - 26.24 The role of fuses 767
 - 26.25 Electrical installation in buildings 767
 - 26.26 Principal components of an electrical installation 767
 - Questions and Problems 769
- 27. THE COST OF ELECTRICITY 771
 - 27.0 Introduction 771
 - 27.1 Tariff based upon energy 772
 - 27.2 Tariff based upon demand 772
 - 27.3 Demand meter 772
 - 27.4 Tariff based upon power factor 774
 - 27.5 Typical rate structures 775
 - 27.6 Demand controllers 775
 - 27.7 Power factor correction 779
 - 27.8 Measuring electrical energy, the watt-hourmeter 782
 - 27.9 Operation of the watt-hourmeter 741
 - 27.10 Meter readout 784
 - 27.11 Measuring three-phase energy and power 785
 - Questions and Problems 785
- 28. DIRECT-CURRENT TRANSMISSION 788
 - 28.0 Introduction 788
 - 28.1 Features of dc transmission 788
 - 28.2 Basic dc transmission system 747
 - 28.3 Voltage, current, and power relationships 790
 - 28.4 Power fluctuations on a dc line 793
 - 28.5 Typical rectifier and inverter characteristic 794
 - 28.6 Power control 795
 - 28.7 Effect of voltage fluctuations 796
 - 28.8 Bipolar transmission line 796
 - 28.9 Power reversal 797
 - 28.10 Components of a dc transmission line 797
 - 28.11 Inductors and harmonic filters on the dc side (6-pulse converter) 798
 - 28.12 Converter transformers 798

- 28.13 Reactive power source 799
- 28.14 Harmonic filters on the ac side 799
- 28.15 Communications link 799
- 28.16 Ground electrode 799
- 28.17 Example of a monopolar converter station 799
- 28.18 Thyristor converter station 800
- 28.19 Typical installations 802
- HVDC Light Transmission System**
- 28.20 Transporting electric power to remote locations, 808
- 28.21 Components of a static generator, 808
- 28.22 Overview of the HVDC light transmission system, 809
- 28.23 Control of active power, 811
- 28.24 Example of a HVDC light transmission system, 812
- Questions and Problems, 814
- 29. TRANSMISSION AND DISTRIBUTION SOLID STATE CONTROLLERS 768
 - TRANSMISSION POWER FLOW CONTROLLERS
 - 29.0 Introduction 768
 - Transmission Power Flow Controllers,**
 - 29.1 Thyristor-controlled series capacitor (TCSC) 817
 - 29.2 Vernier control 819
 - 29.3 Static synchronous compensator 821
 - 29.4 Eliminating the harmonics 824
 - 29.5 Unified power flow controller(UPFC) 824
 - 29.6 Static frequency changer 828
 - DISTRIBUTION CUSTOM POWER PRODUCTS
 - 29.7 Disturbances on distribution systems, 833
 - 29.8 Why PWM converters? 832
 - 29.9 Distribution system 833
 - 29.10 Compensators and circuit analysis 835
 - 29.11 The shunt compensator: principle of operation 835
 - 29.12 The series compensator: principle of operation 841
 - 29.13 Conclusion 844
- 30. HARMONICS 847
 - 30.0 Introduction 847
 - 30.1 Harmonics and phasor diagrams 847
 - 30.2 Effective value of a distorted wave 848
 - 30.3 Crest factor and total harmonic distortion (THD) 849
 - 30.4 Harmonics and circuits 850
 - 30.5 Displacement power factor and total power factor 852
 - 30.6 Non-linear loads 852
 - 30.7 Generating harmonics 853
 - 30.8 Correcting the power factor 855
 - 30.9 Generation of reactive power 856
 - EFFECT OF HARMONICS
 - 30.10 Harmonic current in a capacitor 857
 - 30.11 Harmonic currents in a conductor 858
 - 30.12 Distorted voltage and flux in a coil 858
 - 3-13 Harmonic currents in a 3-phase, 4-wire distribution system 860
 - 30.14 Harmonics and resonance 861
 - 30.15 Harmonic filters 866
 - 30.16 Harmonics in the supply network 867
 - 30.17 Transformers and the K factor 869
 - HARMONIC ANALYSIS
 - 30.18 Procedure of analyzing a periodic wave 871
 - Questions and Problems 875
- 31. PROGRAMMABLE LOGIC CONTROLLERS
 - 31.0 Introduction 879
 - 31.1 Capacity of industrial PLCs 879
 - 31.2 Elements of a control system 880
 - 31.3 Examples of the use of a PLC 883
 - 31.4 The central processing unit (CPU) 886
 - 31.5 Programmng unit 886
 - 31.6 The I/O modules 887
 - 31.7 Structure of the input modules 887
 - 31.8 Structure of the output modules 888
 - 31.9 Modular construction of PLCs 889
 - 31.10 Remote inputs and outputs 889

- 31.11 Conventional control circuits and PLC circuits 892
- 31.12 Security Rule 895
- 31.13 Programming the PLC 895
- 31.14 Programming languages 895
- 31.15 Advantages of PLCs over relay cabinets 896

Modernization of an Industry

- 31.16 Industrial application of PLCs 898
- 31.17 Planning the change 898
- 31.18 Getting to know PLCs 899
- 31.19 Linking the PLCs 901
- 31.20 Programming the PLCs 901
- 31.21 The transparent enterprise 903
- Questions and problems 904

References, 907

Appendixes, 913

AXO Conversion Charts 914

AX1 Properties of Insulating Materials 917

AX2 Electrical, Mechanical and Thermal Properties of Some Common Conductors (and Insulators) 918

AX3 Properties of Round Copper Conductors 919

Answers to Problems 921

Answers to Industrial Application Problems 925

Index 927